

File Edit Draw Scopes Options Tools Circuits

Reset


RUN / Stop

Simulation Speed

Current Speed

Power Brightness


Current Circuit:
Half Adder

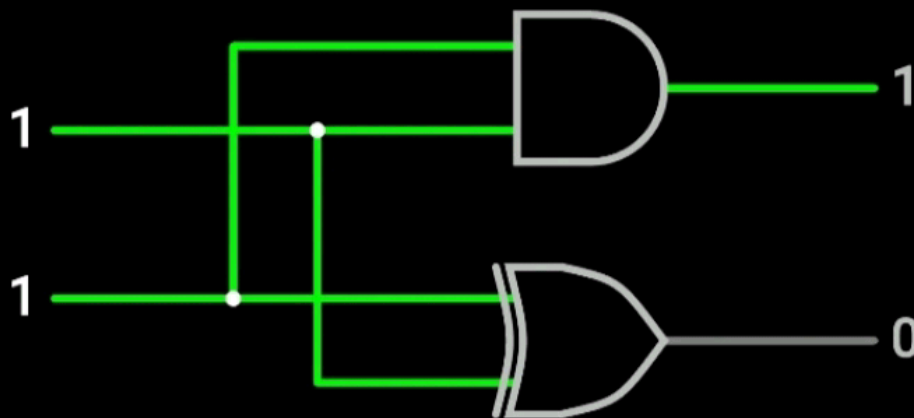

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

t = 101.425 ms
time step = 5 μ s

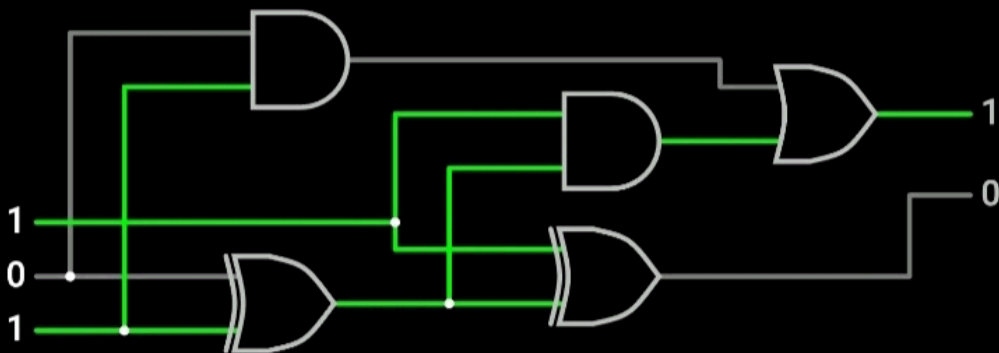File Edit Draw Scopes Options Tools Circuits



A	B	Cin	Sum (S)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

t = 12.58 ms
time step = 5 μ s

Reset

RUN / Stop

Simulation Speed




Current Speed



Power Brightness



Current Circuit:
Full Adder

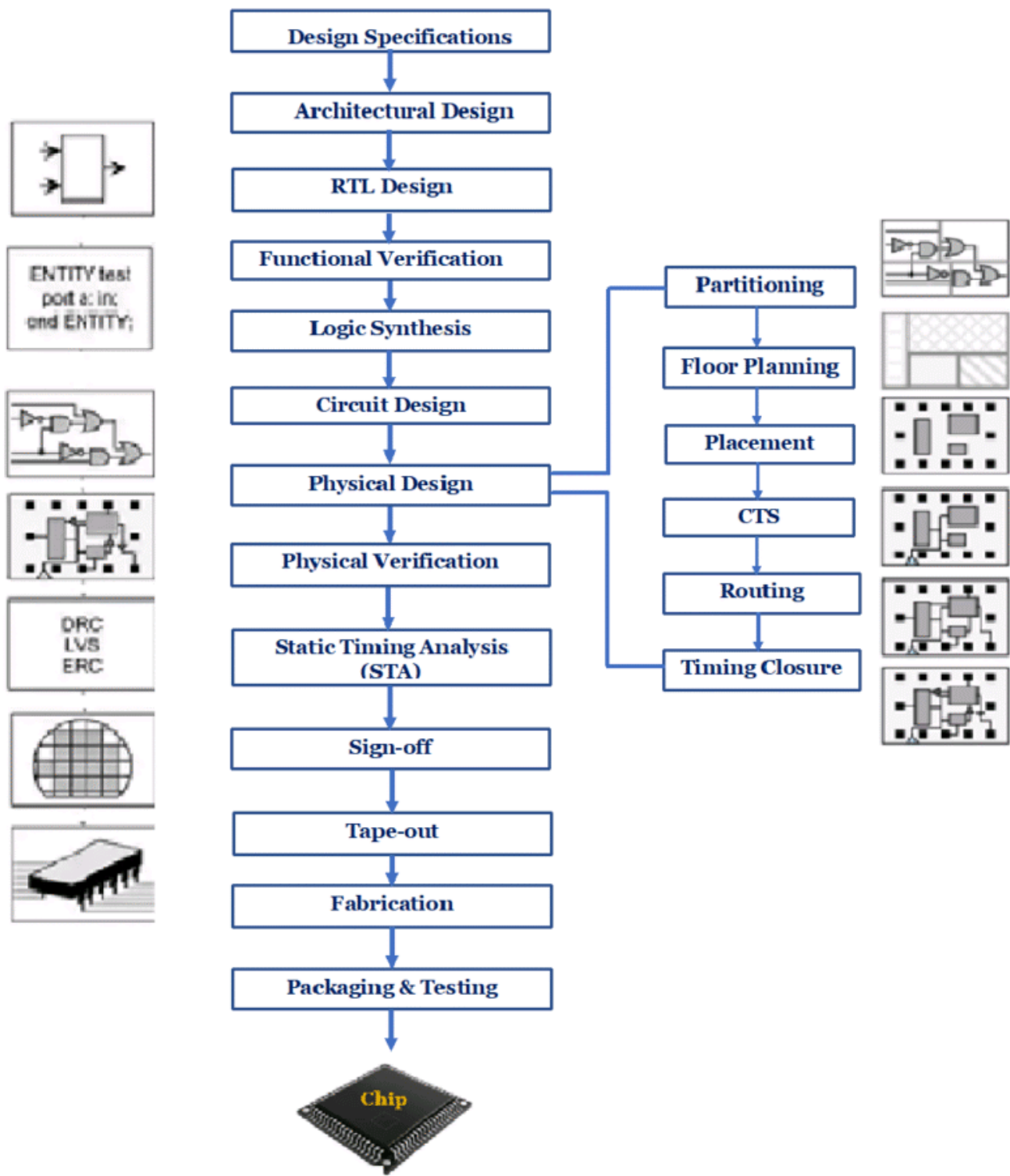


VLSI DESIGN FLOW

Files




A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

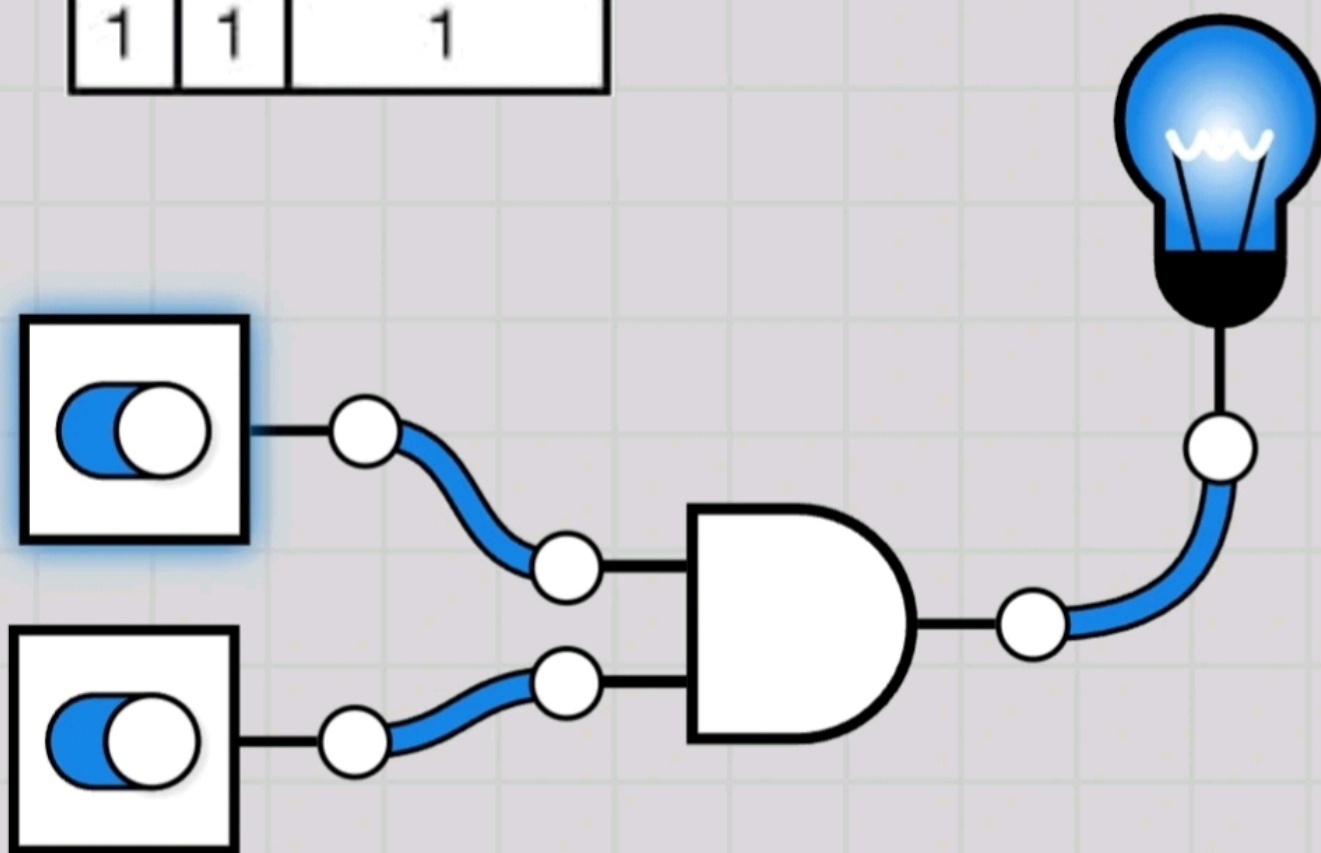

Files




A	B	Output
0	0	1
1	0	1
0	1	1
1	1	0

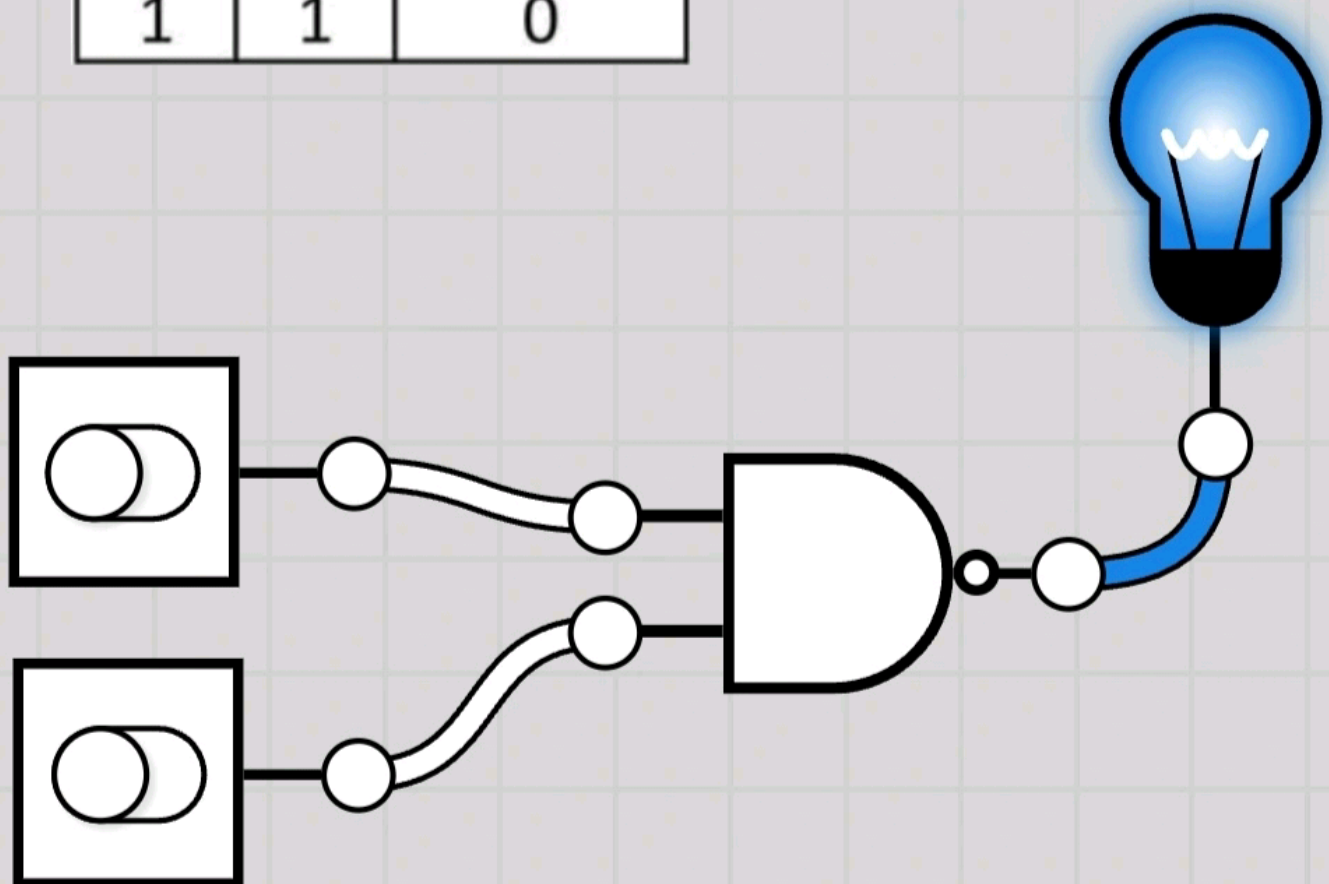

Files




A	B	Output
0	0	1
1	0	0
0	1	0
1	1	0

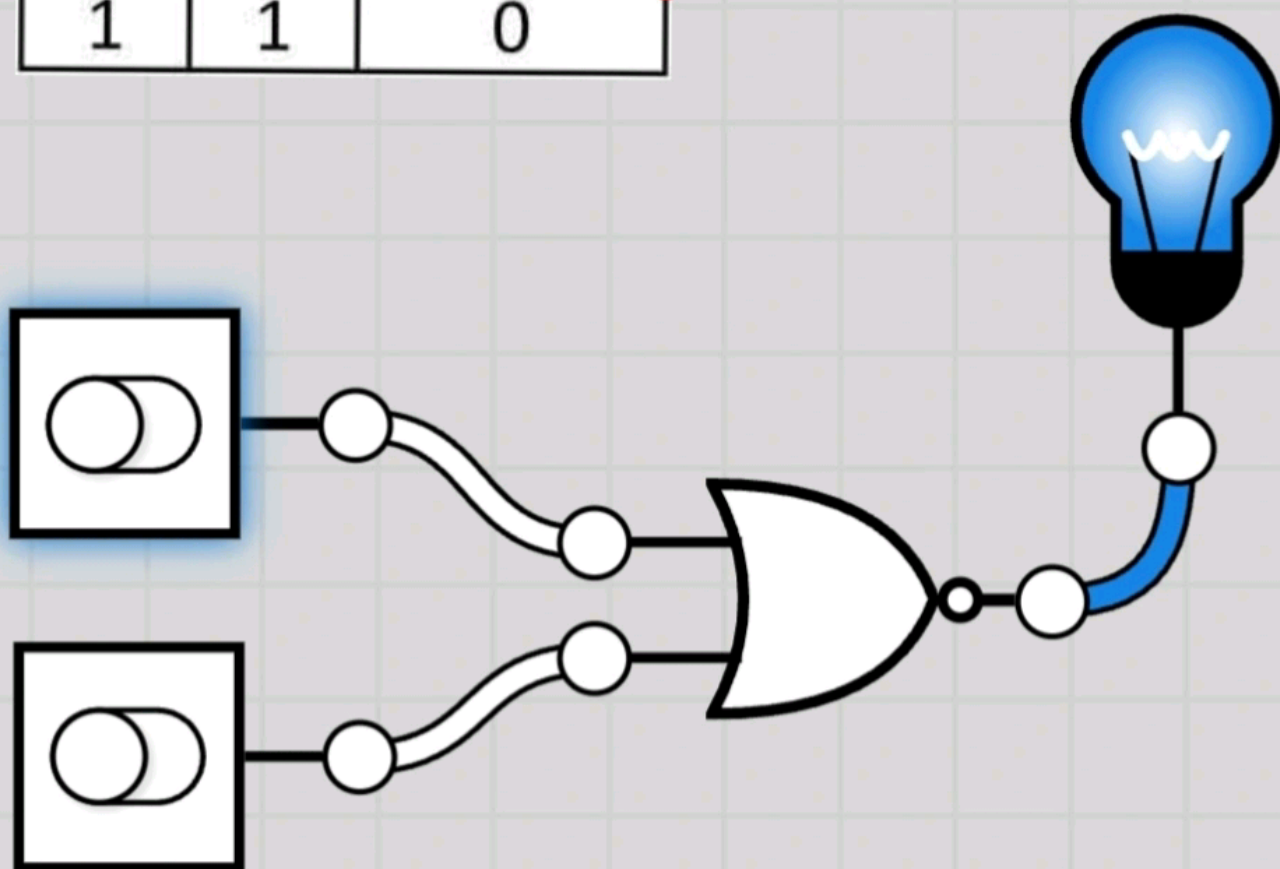

Files




A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

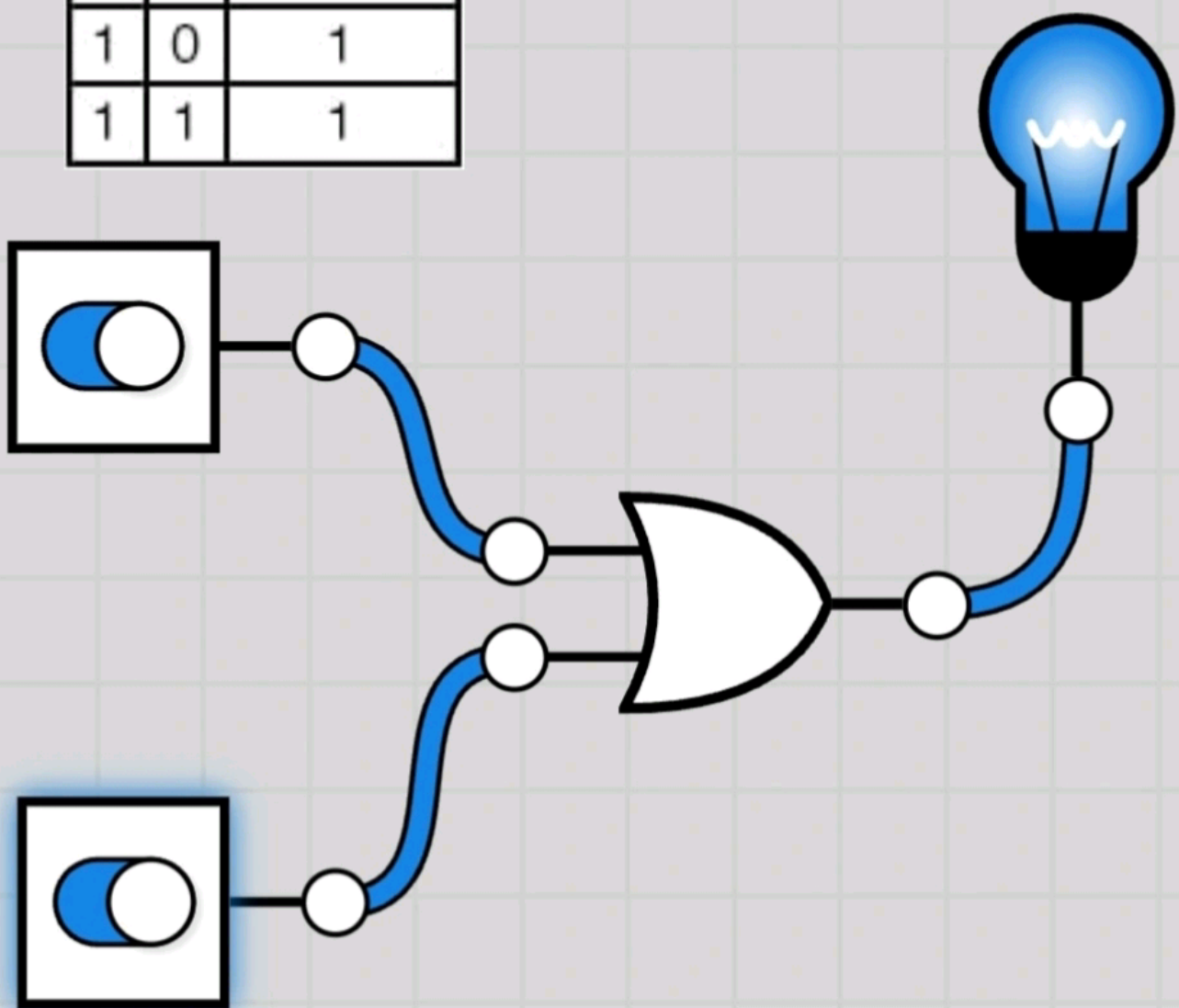



A	B	Q
0	0	0
1	0	1
0	1	1
1	1	0

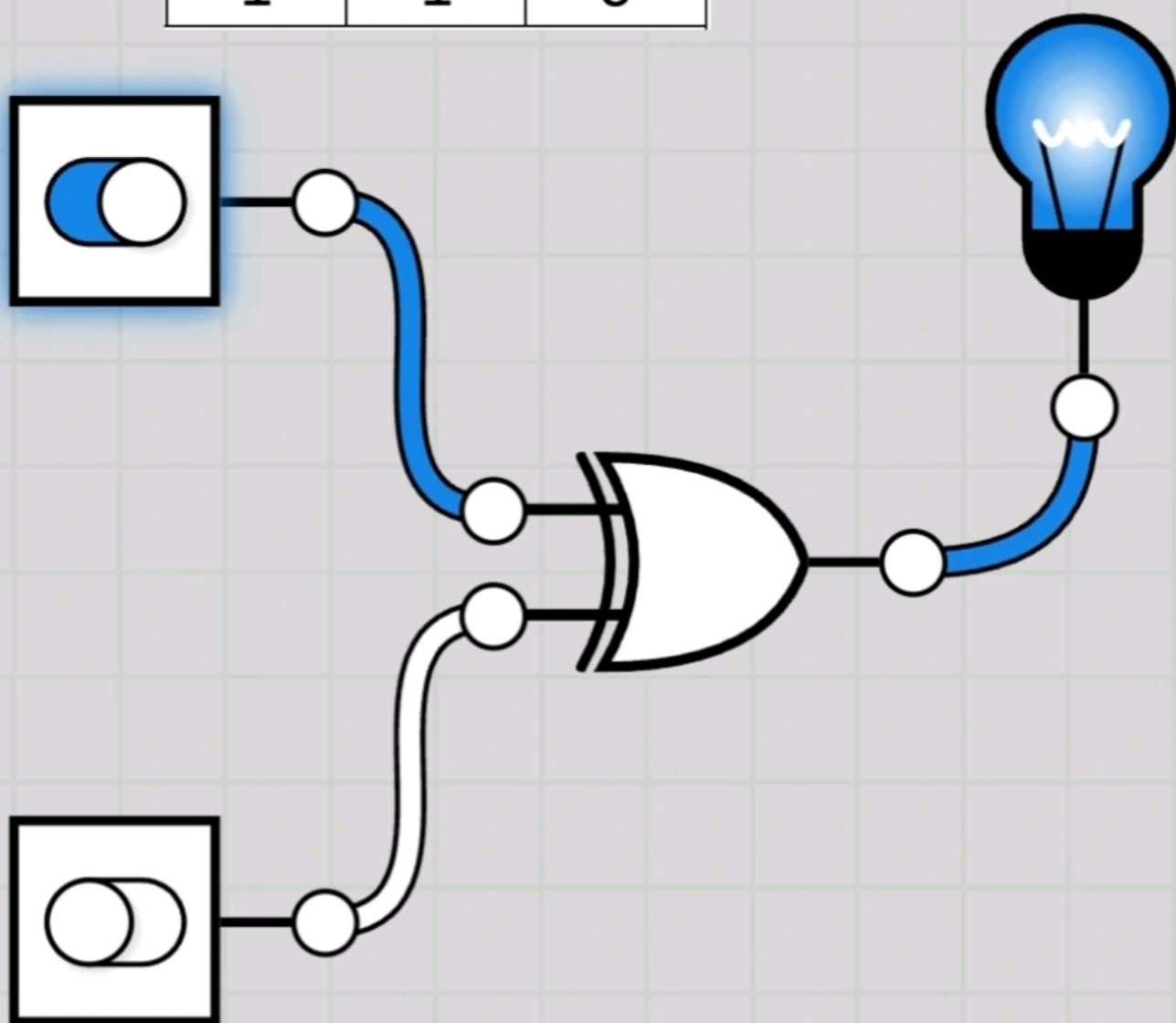

Files



Input	Output
A	Y
0	1
1	0

